Name _____

How Do Electric Circuits Work?

Short Answer

1. Explain the role of conductors in an electric circuit.

2. How does a switch control the flow of electricity in a circuit?

3. Describe what happens in a series circuit if one device fails.

4. Provide an example of a common voltage source.

5. Why is insulation important in electric circuits?

© ReadingDuck.com